

ANALOG ELECTRONICS CIRCUIT

ESC301



Credit: 3

RECTIFIER

- Rectifier circuit converts AC to DC; the process is known as rectification
- Types of rectifier
 - Half wave rectifier
 - Full wave rectifier

Half Wave Rectifier

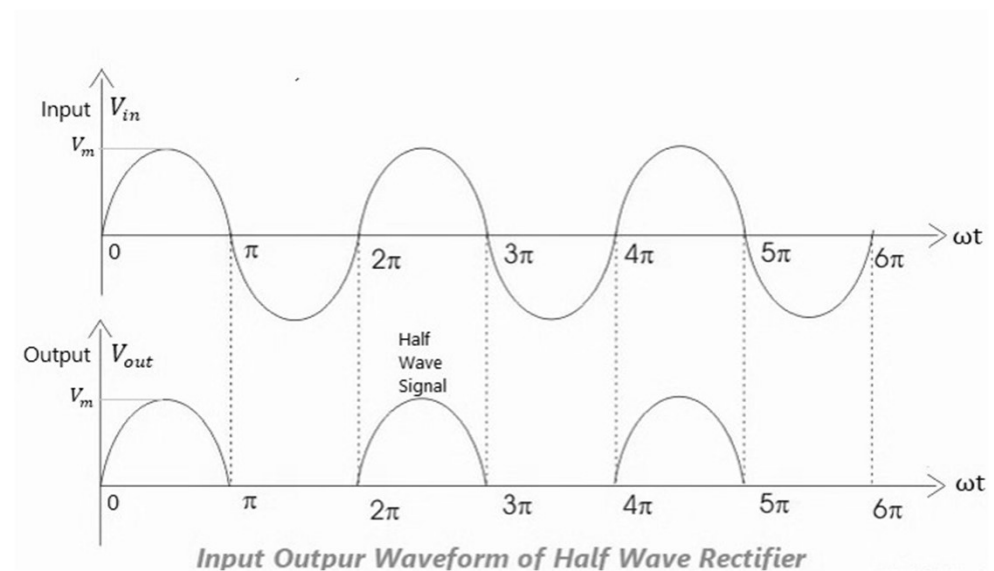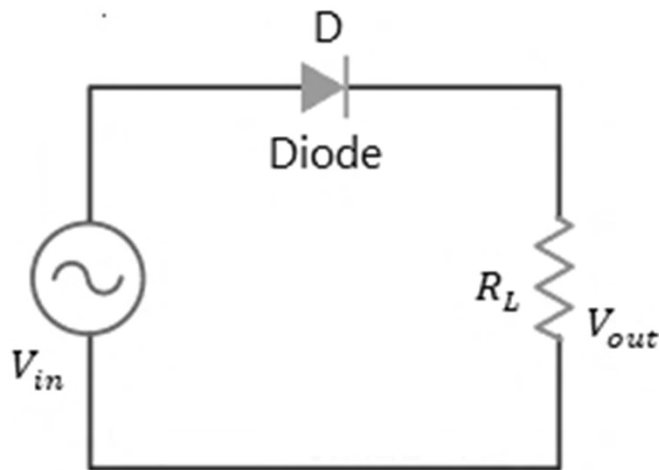- Converts only one-half of the AC input signal to DC output signal.
- Conducts only the positive half cycle of the input AC signal.
- Negative half cycle is suppressed or clipped.
- Therefore, current always flows in one direction through the load after every half-cycle.



- During the positive half-cycle of input A.C. voltage, the diode is forward biased and hence it conducts current.
- During the negative half-cycle, the diode is reverse biased and it conducts no current.
- Therefore, current flows through the diode during positive half-cycles of input A.C. voltage only; it is blocked during the negative half-cycles. In this way, current flows through load R_L always in the same direction. Hence D.C. output is obtained across R_L .
- It may be noted that output across the load is *pulsating D.C.* These pulsations in the output are further smoothened with the help of filter circuits discussed later.

Disadvantages of Half Wave Rectifier

- Power is delivered only for one-half of the cycle; therefore, power output is low.
- The DC output power thus produced is not sufficient to make general power supply.
- The pulsating current in the load contains alternating component whose basic frequency is equal to the supply frequency. Therefore, an elaborate filtering is required to produce steady direct current.

Output frequency of Half Wave Rectifier

- Output frequency is equal to input frequency.
- $f_{out} = f_{in}$


Full Wave Rectifier

- Both half of the input AC signal is passed to the load but they have the same direction.
- Two diodes are put into use alternately.
- Each half cycle activates only one of the two diodes.
- In full-wave rectification, current flows through the load in the same direction for both half-cycles of input A.C. voltage. This can be achieved with two diodes working alternately.
- For the positive half- cycle of input voltage, one diode supplies current to the load and for the negative half-cycle, the other diode does so ; current being always in the same direction through the load.
- Therefore, a full-wave rectifier utilizes both half-cycles of input A.C. voltage to produce the D.C. output.


The following two circuits are commonly used for full-wave rectification: -

- (i) Centre-tap full-wave rectifier (ii) Full-wave bridge rectifier

Full Wave Rectifier

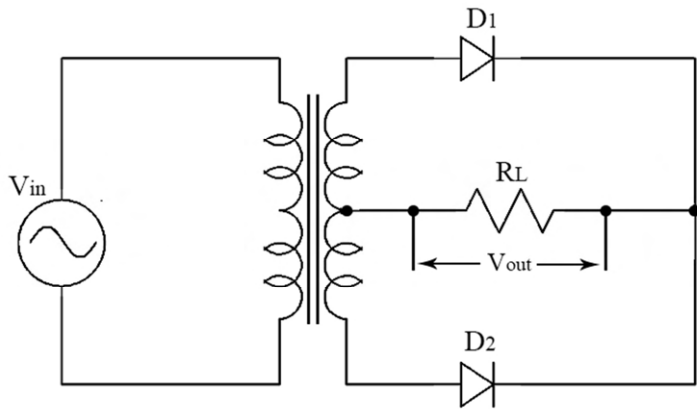

Centre Tapped Full wave Rectifier

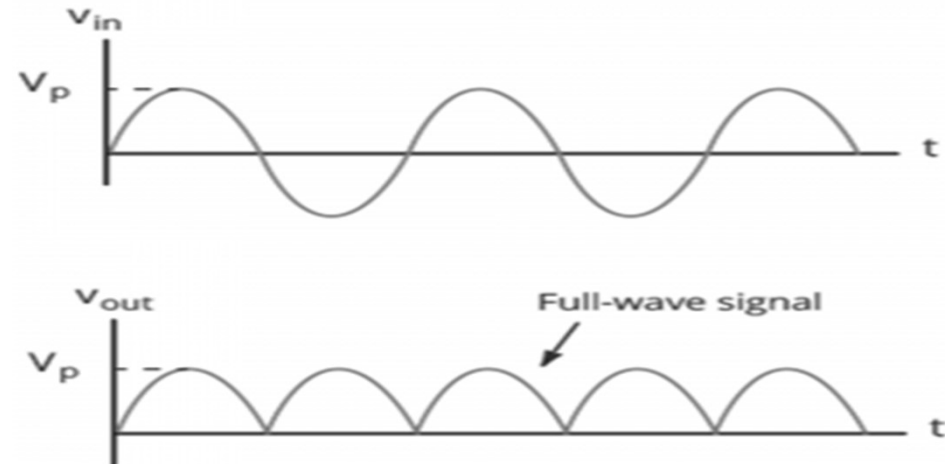

Output frequency of Full Wave Rectifier

- Output frequency is equal to double of input frequency.

- $$f_{out} = 2 f_{in}$$

Full Wave Rectifier- Centre Tapped

- Two diodes are present with centre tap transformer.
- D1 conducts in positive half; D2 conducts in negative half of the input signal.
- Current through load has same direction for both cycle.
- It may be seen that current in the load R_L is in the same direction for both half-cycles of input A.C. voltage. Therefore, D.C. is obtained across the load R_L .



Advantages of Full Wave Rectifier- Centre Tapped

- The D.C. output voltage and load current values are twice than that of a half wave rectifier.
- The ripple factor is much less (0.482) than that of half rectifier (1.21).
- The efficiency is twice (81.2%) than that of half wave rectifier (40.6%).

Disadvantages of Full Wave Rectifier- Centre Tapped

- It is difficult to locate the centre tap on the secondary winding.
- The D.C. output is small as each diode utilizes only one-half of the transformer secondary voltage.
- The diodes used must have high peak inverse voltage.

Full Wave Rectifier- Bridge Rectifier

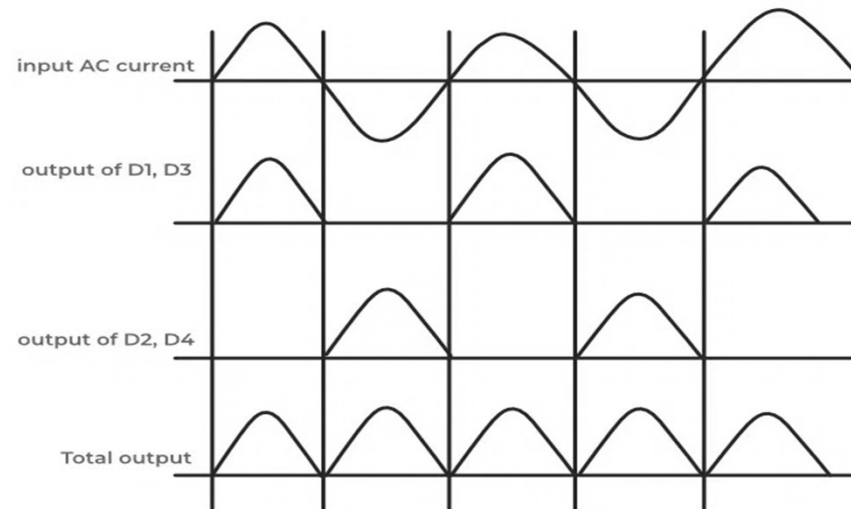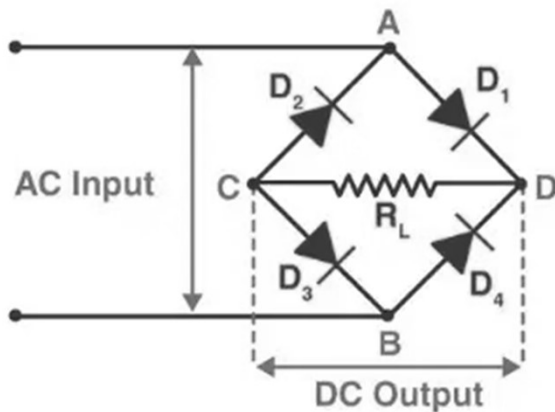

waveforms-of-bridge-rectifier

- Four diodes are present which form a bridge.
- D_1 and D_3 conduct in first half while D_2 and D_4 are off.
- D_2 and D_4 conduct in second half while D_1 and D_3 are off.
- Current through load has same direction for both cycle.